

[20]

6- Inputs  $X_i$  and  $Y_i$  of each full adder in a 4-bit arithmetic circuit have digital logic specified by the Boolean functions

$$X_i = A_i \quad Y_i = B_i' S + B_i C_{in}'$$

where  $S$  is a selection variable,  $C_{in}$  is the input carry, and  $A_i$  and  $B_i$  are input data for stage  $i$ .

a-Determine the arithmetic operation performed for each of the four combinations of  $S$  and  $C_{in}$ : 00, 01, 10, and 11.


b-Draw the logic diagram for the 4-bit circuit, using full adders and multiplexers.

a)

| $S$ | $C_{in}=0$  | $C_{in}=1$       |
|-----|-------------|------------------|
| 0   | $F = A + B$ | $F = A + 1$      |
| 1   | $F = A - 1$ | $F = A + B' + 1$ |

8 P.

b)

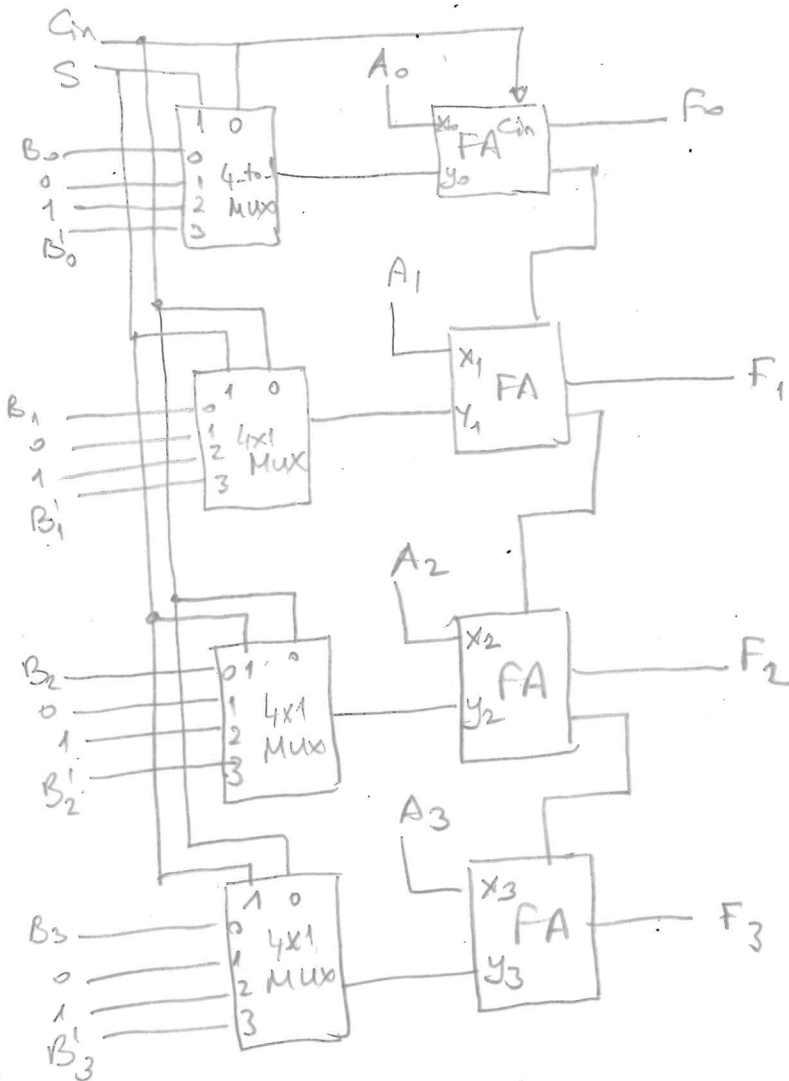

12 P.

Good Luck...